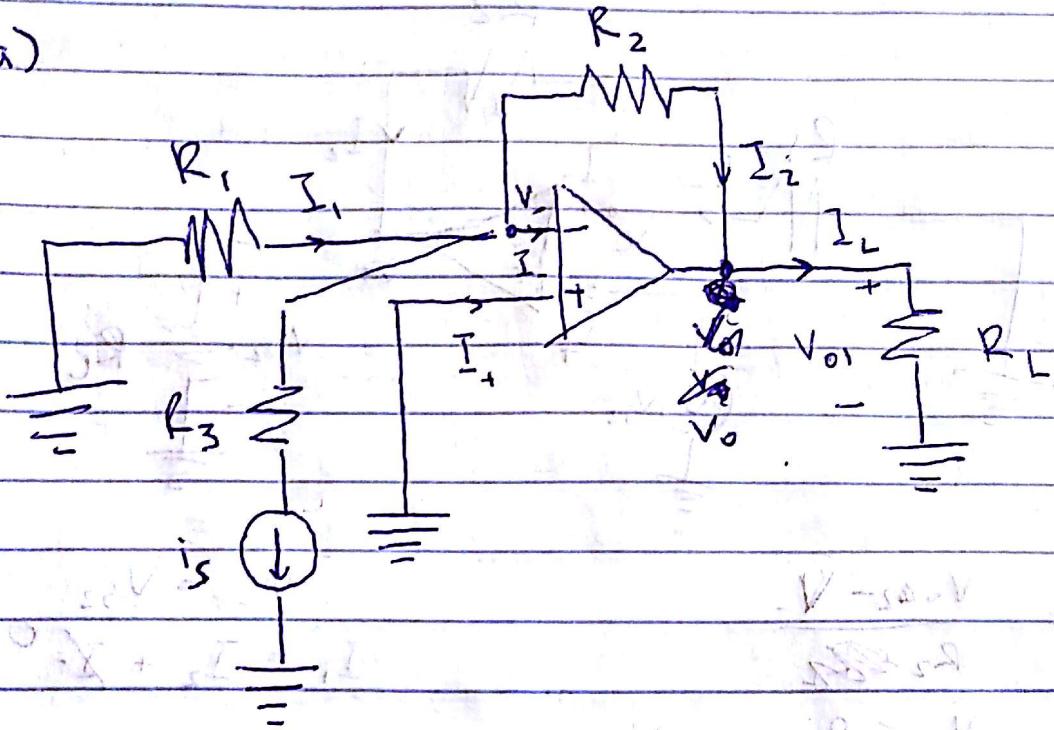


2a)



$$I_1 = I_2 + i_s \quad V_- = V_+ = 0$$

$$I_1 = \frac{V - 0}{R_1} = \frac{0}{R_1} = 0 \quad I_- = I_+ = 0$$

$$I_2 = -i_s \quad V_{o1} = I_L R_L$$

~~$$I_2 = \frac{V_o - V_-}{R_2} = \frac{V_o - 0}{R_2} = \frac{V_o}{R_2}$$~~

$$I_2 = I_L$$


$$I_1 = \frac{V - 0}{R_1} = 0 \quad I_2 = \frac{V_{o1} - V_-}{R_2} = \frac{V_o - 0}{R_2} = \frac{V_o}{R_2}$$

$$I_L = \frac{0 - V_o}{R_L} = \frac{-V_o}{R_L} = \frac{V_o}{R_2}$$

$$V_o = R_2 I_L = -R_2 i_s$$

$$V_{o1} = -R_2 i_s$$

b)

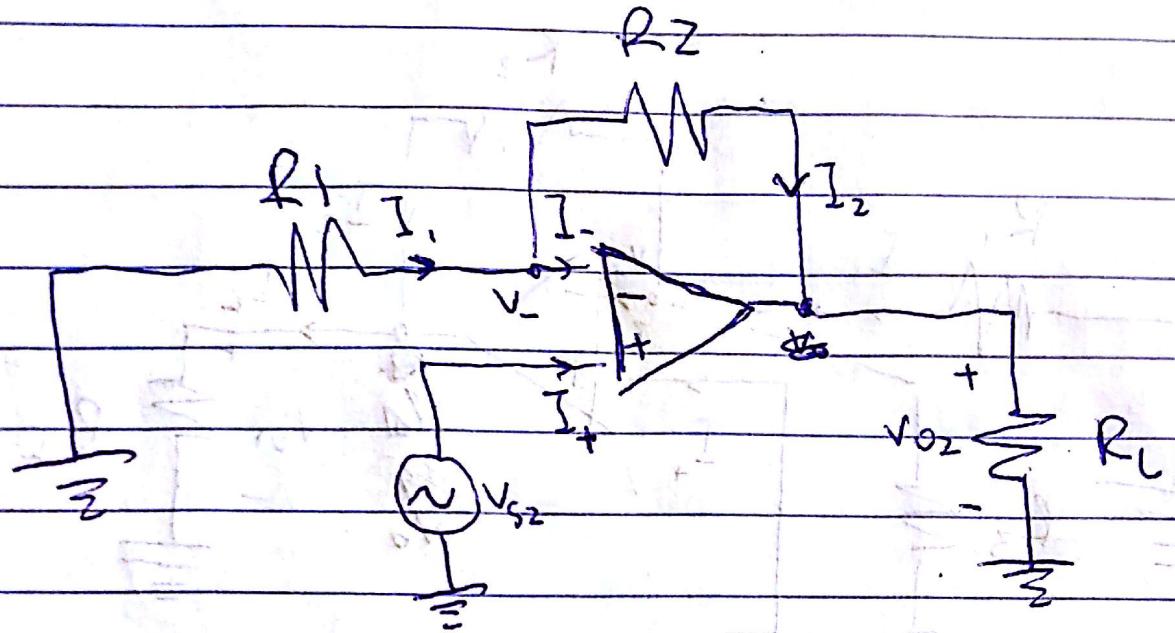

$$I_2 = \frac{V_{O2} - V_-}{R_2 + R_L}$$

$$V_- = V_{S2}$$

$$I_1 = I_2 + I_-^0$$

$$I_1 = \frac{V_- - 0}{R_1} = \frac{V_{S2}}{R_1}$$


~~$$V_{O2} = I_2 (R_2 + R_L) + V_{S2}$$~~

~~$$R_2 (I_2 (R_2 + R_L))$$~~

~~$$V_{O2} / R_2 = V_- - V_{S2}$$~~

$$\frac{V_{O2} - V_{S2}}{R_2} \rightarrow \frac{V_{S2}}{R_1}$$
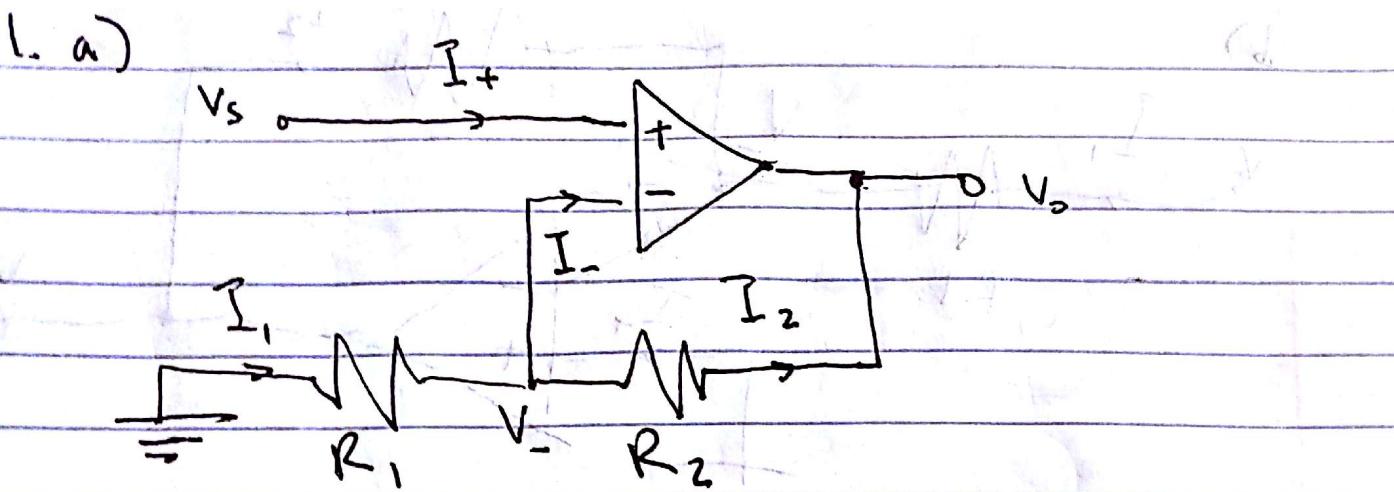
$$V_{O2} = V_{S2} \left( \frac{R_2}{R_1} + 1 \right)$$



$$I_- = I_+ = 0 \quad I_1 = I_- + I_2 \quad I_1 = I_2$$

$$V_- = V_s$$

$$I_2 = \frac{V_- - V_0}{R_2} = \frac{V_s - V_0}{R_2}$$


$$\frac{0 - V_-}{R_1} = I_1 \quad \frac{-V_-}{R_1} = \frac{V_s - V_0}{R_2}$$

$$\frac{-V_s}{R_1} = \frac{V_s - V_0}{R_2}$$

$$V_s + \frac{V_s R_2}{R_1} = V_0$$

$$V_0 = V_s \left( 1 + \frac{R_2}{R_1} \right)$$

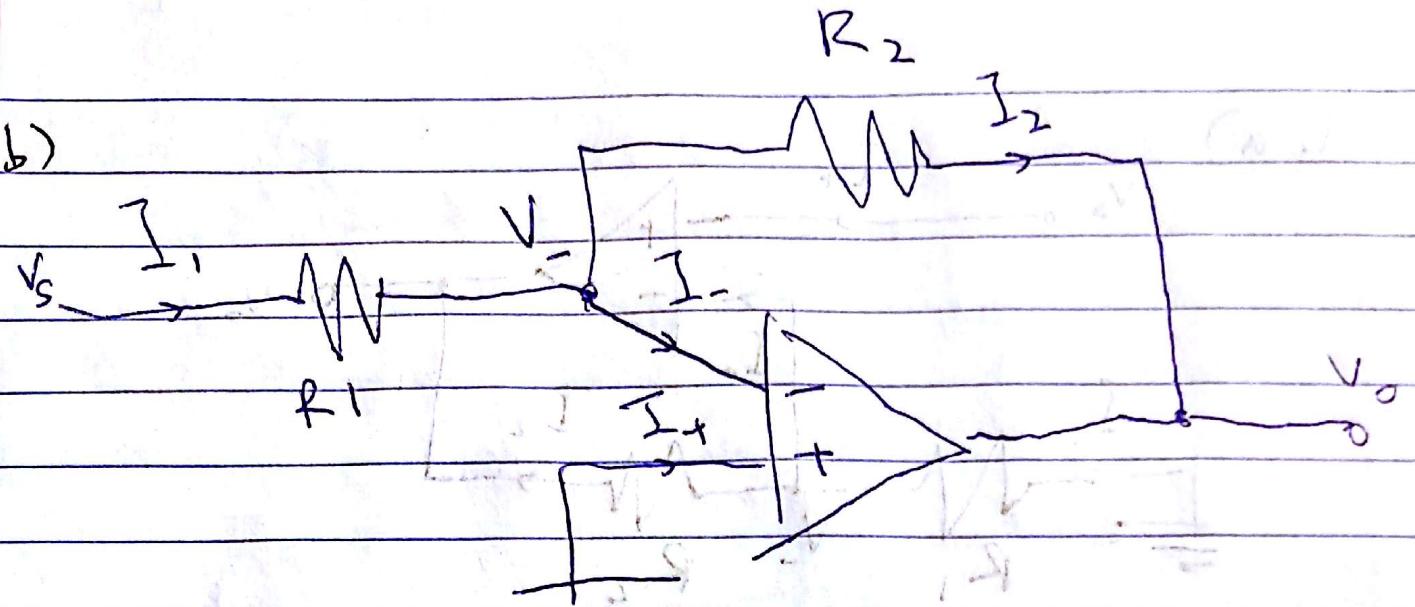the amplifier is now inverting because if  $V_s$  is positive,  $V_0$  stays positive.



$$V_- = 0 \quad V_+ = 0$$

$$I_1 = I_- + I_2 = 0 \quad I_1 = I_2$$

$$I_1 = \frac{V_s - V_-}{R_1} = \frac{V_s}{R_1}$$

$$I_2 = \frac{V_- - V_o}{R_2} = -\frac{V_o}{R_2}$$


$$\frac{V_s}{R_1} = -\frac{V_o}{R_2}$$

$$V_o = -\frac{R_2}{R_1} V_s$$

amplifier is inverting because  $V_o$  switches the sign of  $V_s$ , therefore inverting it

switches state in addition

c)

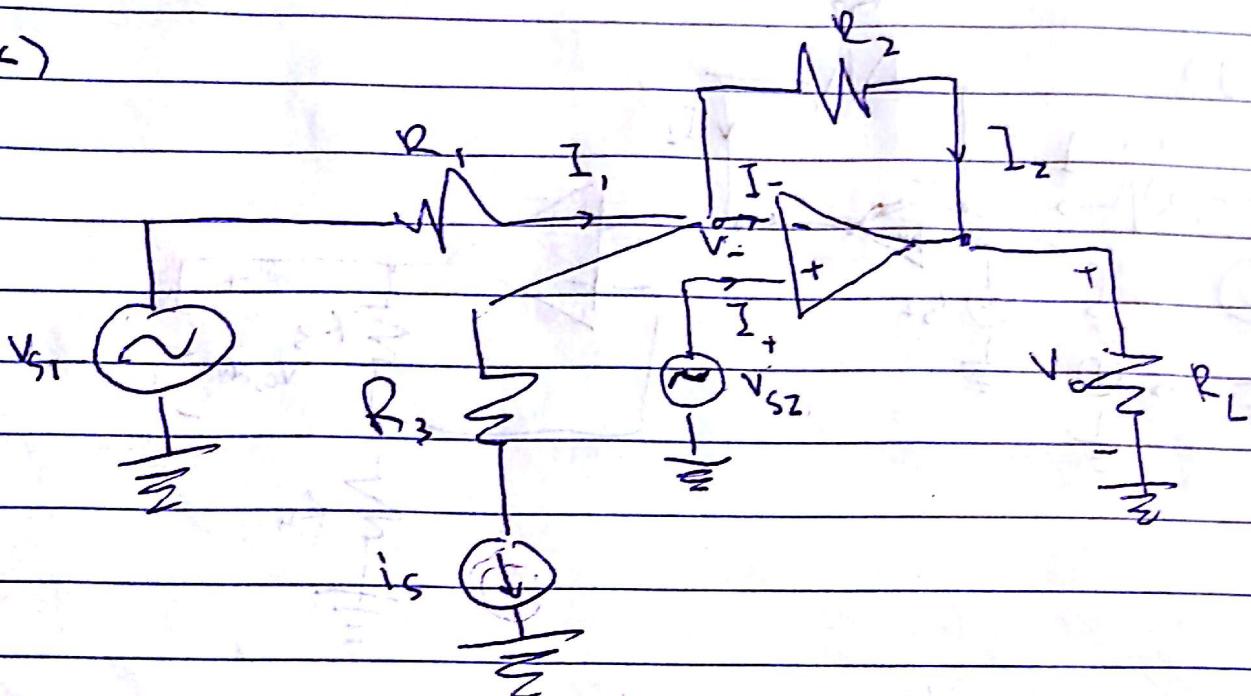


$$I_1 = I_{-}^0 + I_2 + i_s \quad I_1 = I_2 + i_s$$
$$V_{-} = V_{+} - V_{S2}$$

$$I_1 = \frac{V_{-} - V_{S1}}{R_1} \quad I_2 = \frac{V_o - V_{-}}{R_2}$$

$$\frac{V_o - V_{S2}}{R_2} = \frac{V_{S2} - V_{S1}}{R_1} + i_s$$
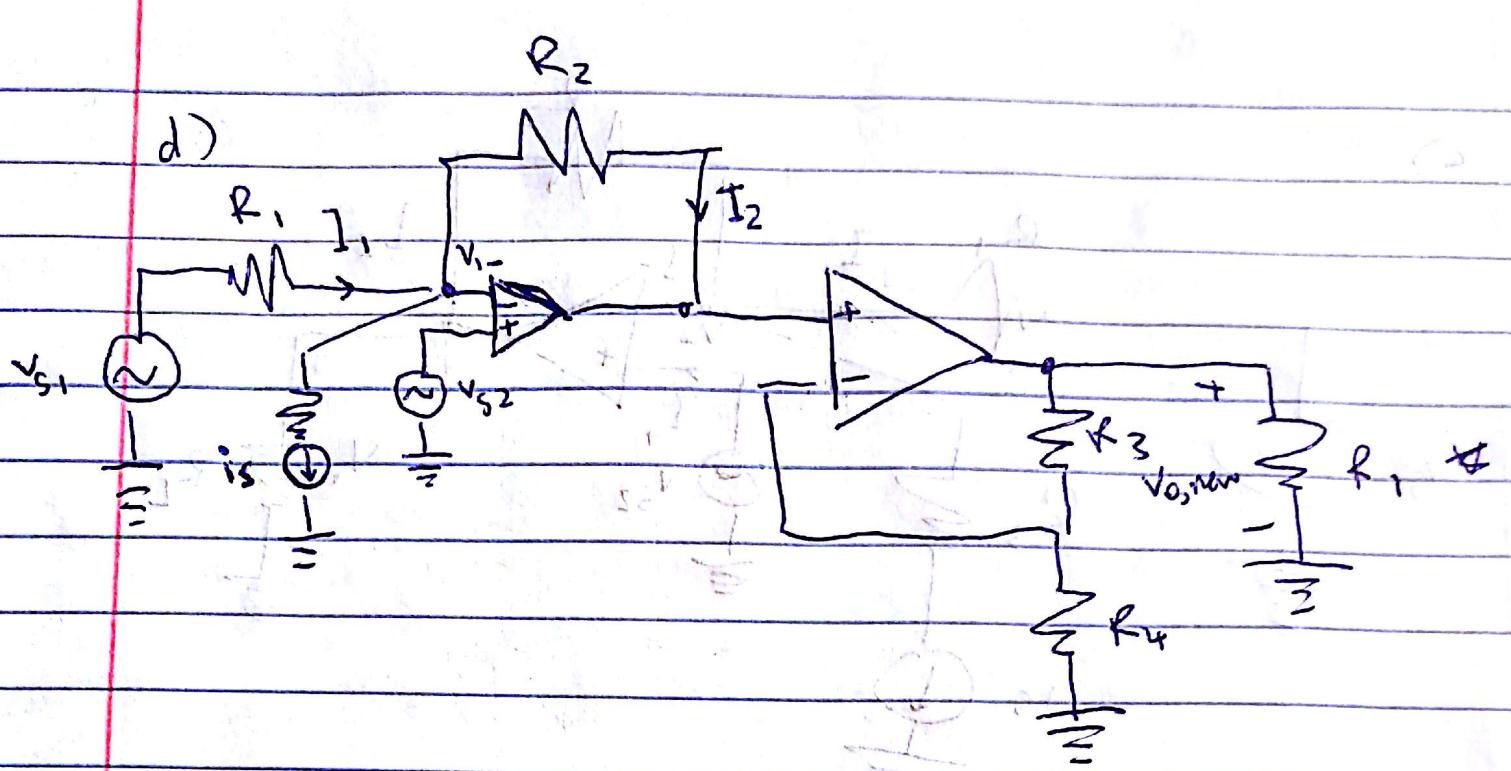
$$V_o = R_2 \left( \frac{V_{S2} - V_{S1}}{R_1} + i_s \right) + V_{S2}$$



$$V_o = V_+ = V_-$$


$$V_- = \frac{V_o, \cancel{new}}{R_3 + R_4} \cdot R_3$$

$$V_o, \cancel{new} = \frac{V_o (R_3 + R_4)}{R_3}$$

$V_o$  does not change

$V_o, \cancel{new}$  does depend on  $R_L$

$$3. R_1 \parallel (R_2 + R_3) + R_4$$

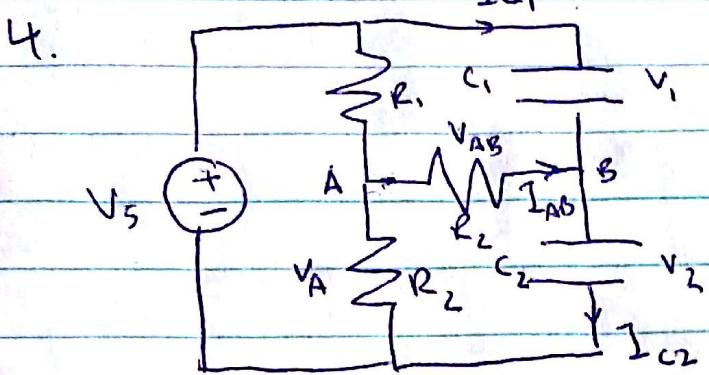

$$I_{C1} = 0, I_{C2} = 0$$

$$I_{AB} = 0$$

$$V_{AB} = 0 \quad \cancel{V_A = V_B}$$

$$V_A = \frac{R_2}{R_1 + R_2} V_s$$

$$V_2 = \cancel{R_2} V_A - V_{AB} = 0$$

$$= \frac{R_2}{R_1 + R_2} V_s = \frac{1}{3} \times 3 = 1$$

$$V_1 = V_s - V_2$$

$$V_1 = \frac{R_1}{R_1 + R_2} V_s = \frac{2}{3} \times 3 = 2$$

$$5. \frac{V_A - V_B}{R_1} = \frac{V_1 - V_A}{R_2} + \frac{-V_A}{R_2}$$

$$\frac{V_A}{R_1} - \frac{V_B}{R_1} = \frac{V_1}{R_2} - \frac{V_A}{R_2} - \frac{V_A}{R_2}$$

$$\frac{V_1}{2} = V_A \left( \frac{1}{2} + \frac{1}{2} + 1 \right) - V_B$$


$$\frac{V_1}{2} = 2V_A - V_B$$

$$\frac{V_2 - V_s}{R_2} = \frac{V_A - V_B}{R_1}$$

$$\frac{V_2}{R_2} + \frac{V_s}{R_2} = \frac{V_A}{R_1} - \frac{V_B}{R_1}$$

$$\frac{V_2}{2} = V_B \left( \frac{1}{2} + 1 \right) - V_A$$

(e. a)

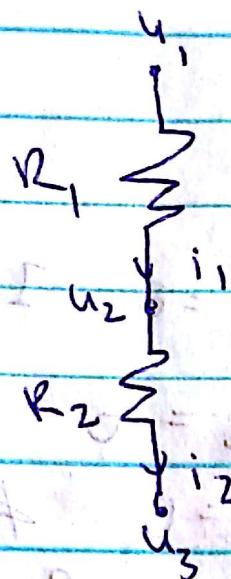

b)


$$\begin{aligned} u_1 &= i_1 R_1 \\ u_2 &= i_1 R_1 \\ u_3 &= i_2 R_2 \end{aligned}$$

$$\begin{bmatrix} 1 & -1 & 0 \\ 0 & 1 & -1 \end{bmatrix}$$


c)

$$\begin{bmatrix} I_{S1} \\ I_{S2} \\ -I_{S1} - I_{S2} \end{bmatrix}$$

$$7. a) \frac{1}{5} \times 20 = 4$$

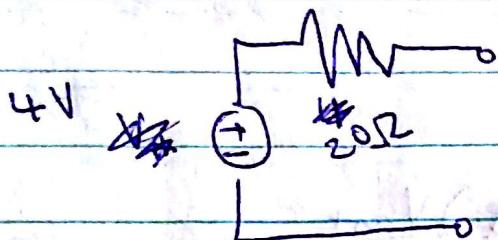

b)

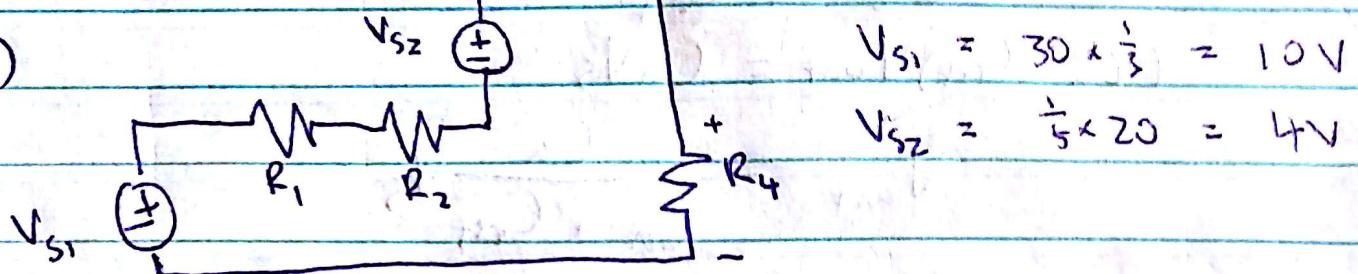

$$V_{S1} = 30 \times \frac{1}{3} = 10V$$

$$V_{S2} = \frac{1}{5} \times 20 = 4V$$

c)

$$14 \times \frac{10}{30 + 10 + 20 + 10} = \frac{140}{70} = 2V$$

8.

$$I_{AB} = \frac{R_1}{R_1 + R_2 + (R_3 \parallel R_4)} I_s$$

$$V_m = R_2 I_{AB} = \frac{R_1}{R_1 + R_2 + (R_3 \parallel R_4)} I_s R_2$$

$$R_{th} = R_2 \parallel (R_1 + (R_3 \parallel R_4))$$

9. a)

$$R_y = \frac{\rho_y L}{A}$$

$$R_x = \frac{\rho_x W}{A}$$

$$10. a) C = \epsilon \frac{Wx}{d}$$

$$b) Q_1 = Q_a + Q_{ref} = C_a V_s$$

$$Q_2 = Q_a + Q_{ref} = ((C_a + C_{ref}) V_{out})$$

$$Q_2 = Q_1$$

$$(C_a + C_{ref}) V_{out} = C_a V_s$$

$$V_{out} = \frac{C_a}{C_a + C_{ref}} V_s$$

$$c) \cancel{C_a V_s + C_{ref} V_{out}[k-1]} = \cancel{C_a V_s + C_{ref} V_{out}[k-1]}$$

$$(C_a V_s + C_{ref} V_{out}[k-1]) = (C_a V_{out}[k] + C_{ref} V_{out}[k])$$

$$V_{out}[k] = \frac{(C_a V_s + C_{ref} V_{out}[k-1])}{(C_a + C_{ref})}$$

11. Bruce Lau 26310857